

Exercises
Chapter 10.1

1. $v_{in}(t) = 10 \cos(2t + 40^\circ)$

Input frequency = 2 rad/sec , so output

frequency must be $\underline{\underline{2 \text{ rad/sec}}}$

2. $v_{in}(t) = 10 \cos(2t + 40^\circ)$

$$\left| \frac{V_{out}}{V_{in}} \right| = 0.5, \quad \text{Input phase} - \text{output phase} = 20^\circ$$

(a) 2 rad/sec (same as input)

(b) $\left| \frac{V_{out}}{V_{in}} \right| = 0.5 \Rightarrow |V_{out}| = 0.5 |V_{in}| = 0.5 (10)$

$$|V_{out}| = 5 \text{ V}$$

(c) $40^\circ - \phi = 20^\circ \Rightarrow \phi = 20^\circ$

↑
input phase

Note: Output wave form is, thus:

$$v_{out}(t) = 5 \cos(2t + 20^\circ)$$

chapter 10.2

Exercises

1.

$$(a) \frac{3}{\sqrt{2}} (1+j)$$

$$(b) 5(-1+j)$$

$$(c) j2.5$$

$$(d) -6$$

2.

$$(a) 2\sqrt{2} e^{-j45^\circ}$$

$$(b) 3 e^{-j90^\circ}$$

$$(c) 6$$

$$(d) \sqrt{10} e^{j18.4^\circ}$$

3.

$$(a) \frac{-j}{2(j+1)} = \frac{1 \angle -90^\circ}{2\sqrt{2} \angle 45^\circ} = \frac{1}{2\sqrt{2}} \angle -135^\circ = \underline{\underline{\frac{1}{2\sqrt{2}} e^{j(-135^\circ)}}}$$

$$(b) \frac{2-j2}{4+j4} = \frac{2\sqrt{2} \angle -45^\circ}{4\sqrt{2} \angle +45^\circ} = \underline{\underline{\frac{1}{2} \angle -90^\circ}} = \underline{\underline{\frac{1}{2} e^{j(-90^\circ)}}} = \underline{\underline{-\frac{j}{2}}}$$

$$(c) 2 e^{j45^\circ} \frac{2}{j+1} = 2 \angle 45^\circ \frac{2}{\sqrt{2} \angle 45^\circ} = \frac{4}{\sqrt{2}} = \underline{\underline{2\sqrt{2}}}$$

$$(d) j + \frac{2}{j} = j + \frac{2}{1 \angle 90^\circ} = j + 2 \angle -90^\circ = j - j2 = -j = \underline{\underline{e^{-j90^\circ}}}$$

Chapter 10.2
Exercises

- 4.
- (a) $3 \angle -60^\circ$ or $3e^{-j60^\circ}$
 - (b) $-2 \angle 45^\circ = 2 \angle 225^\circ$ or $2e^{j225^\circ}$
 - (c) $\sin(6t) = \cos(6t - 90^\circ) \Rightarrow 1 \angle -90^\circ$ or $1e^{-j90^\circ}$
 - (d) $7 \angle 0^\circ = 7$ or $7e^{j0^\circ}$

- 5.
- (a) $5\sqrt{2} \cos(100t - 45^\circ)$
 - (b) $3 \cos(3t + \pi)$
 - (c) $2 \cos(\pi t - 30^\circ) + 4 \cos(4t + 20^\circ)$

1.

$$u(t) = 2 \cos(3t)$$

$$\text{let } u(t) = 2e^{j3t}, \quad y(t) = \underline{Y} e^{j3t} \Rightarrow \frac{dy}{dt} = j3 \underline{Y} e^{j3t}$$


$$2 \frac{dy}{dt} + 6y(t) = u(t) \Rightarrow 2 [j3 \underline{Y} e^{j3t}] + 6 [\underline{Y} e^{j3t}] = 2e^{j3t}$$

$$j6 \underline{Y} e^{j3t} + 6 \underline{Y} e^{j3t} = 2e^{j3t}$$

$$\underline{Y} = \frac{2}{6 + j6} = \frac{2}{6\sqrt{2} \angle 45^\circ} = \frac{1}{3\sqrt{2}} \angle -45^\circ$$

$$\underline{y(t)} = \underline{\frac{1}{3\sqrt{2}} \cos(3t - 45^\circ)}$$

2.

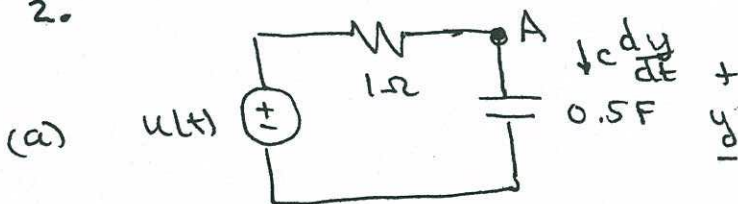

KCL at A:

$$\frac{u - y}{1\Omega} = 0.5F \frac{dy}{dt}$$

$$\frac{dy}{dt} + 2y = 2u$$

(b) $u(t) = 3 \cos(2t) \Rightarrow \text{let } u(t) = 3e^{j2t} \quad \& \quad y(t) = \underline{Y} e^{j2t}$

$$(j2) \underline{Y} e^{j2t} + 2 \underline{Y} e^{j2t} = 2(3e^{j2t})$$

$$\underline{Y} = \frac{6}{2 + j2} = \frac{6}{2\sqrt{2} \angle 45^\circ} = \frac{3}{\sqrt{2}} \angle -45^\circ \Rightarrow \underline{y(t)} = \underline{\underline{\frac{3}{\sqrt{2}} \cos(2t - 45^\circ)}}$$


Exercises

Chapter 10.4.

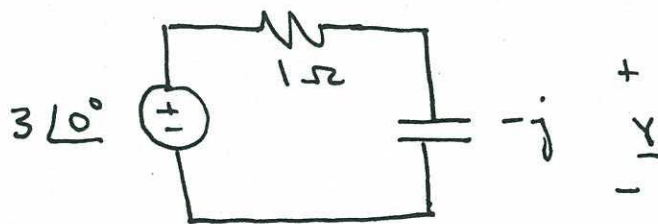1. We did this problem in exercise 2 of chapter 10.3, but let's do it differently here. (This approach won't be formally introduced until chapter 10.5)

• At a frequency of 2 rad/sec, the capacitor impedance is $\frac{1}{j(2)(0.5)} = -j$.

• Substitute the frequency-domain representations of the input and the capacitor into the circuit:



Now use voltage divider formula to find

\underline{Y} :


$$\underline{Y} = 3\angle 0^\circ \left(\frac{-j}{1-j} \right) = 3\angle 0^\circ \left(\frac{1\angle -90^\circ}{\sqrt{2}\angle -45^\circ} \right)$$

$$\underline{Y} = \frac{3}{\sqrt{2}} \angle -45^\circ \Rightarrow \underline{y(t)} = \underline{\underline{\frac{3}{\sqrt{2}} \cos(2t - 45^\circ)}}$$

Exercises
Chapter 10.4

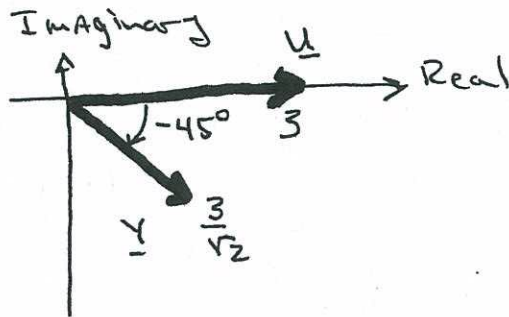2.

$$\underline{U} = 3 \angle 0^\circ, \quad \underline{Y} = \frac{3}{\sqrt{2}} \angle -45^\circ$$



3.

$$2 \cos 4t \quad \left[\text{Circuit: Capacitor } \frac{1}{8} \text{ F} \right] \Rightarrow Z = \frac{1}{j\omega C} = \frac{1}{j(4)\frac{1}{8}} = \underline{\underline{-j2\Omega}}$$

$$2 \cos 4t \quad \left[\text{Circuit: Inductor } 2 \times 10^{-3} \text{ H} \right] \Rightarrow Z = j\omega L = j(4)(2 \times 10^{-3}) = \underline{\underline{j8 \text{ m}\Omega}}$$

$$\left[\text{Circuit: Resistor } 5 \text{ k}\Omega \right] \Rightarrow \underline{\underline{Z = 5 \text{ k}\Omega}}$$

4.


$$3 \cos 8t \quad \left[\text{Circuit: Capacitor } \frac{1}{8} \text{ F} \right] \Rightarrow Z = \frac{1}{j\omega C} = \underline{\underline{-j1\Omega}}$$

$$3 \cos 8t \quad \left[\text{Circuit: Inductor } 2 \text{ mH} \right] \Rightarrow Z = j\omega L = j(8)(2 \times 10^{-3}) = j16 \text{ m}\Omega$$



$5 \text{ k}\Omega$ resistor's impedance is $5 \text{ k}\Omega$, independent of frequency

Exercises
Chapter 10.5

1.


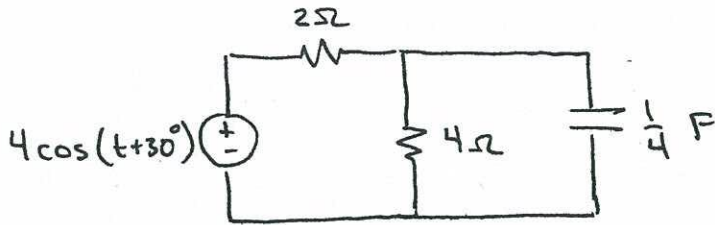


$\omega = 1 \text{ rad/sec}$

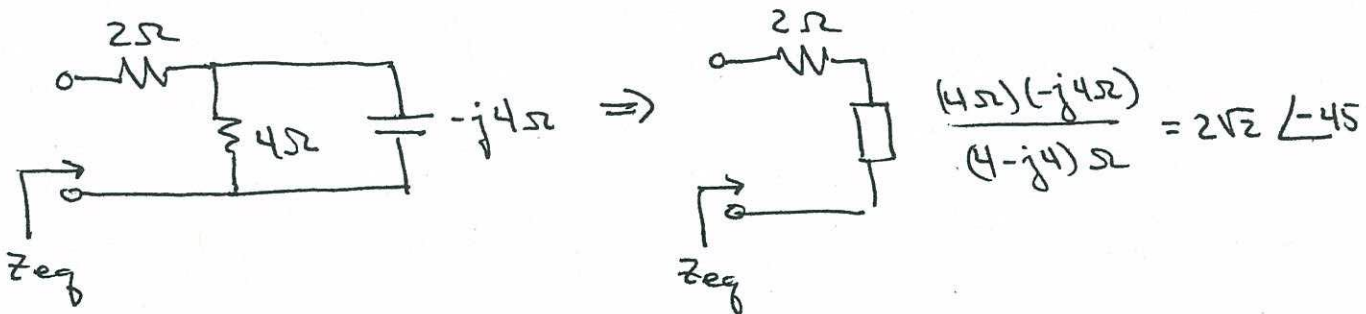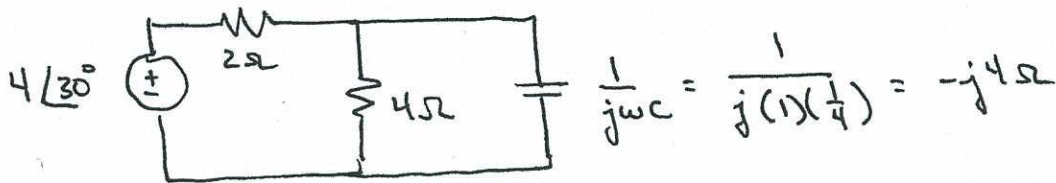


$$Z_{eq} = 2 \Omega + 2\sqrt{2} \angle -45^\circ = 2 + (2 - j2) = \underline{4 - j2} \Omega = \underline{2\sqrt{5} \angle -26.6^\circ}$$

2.

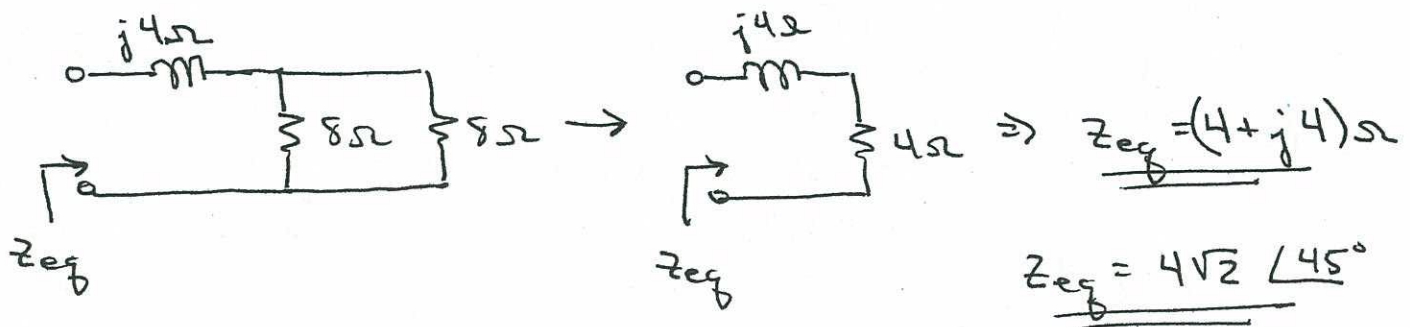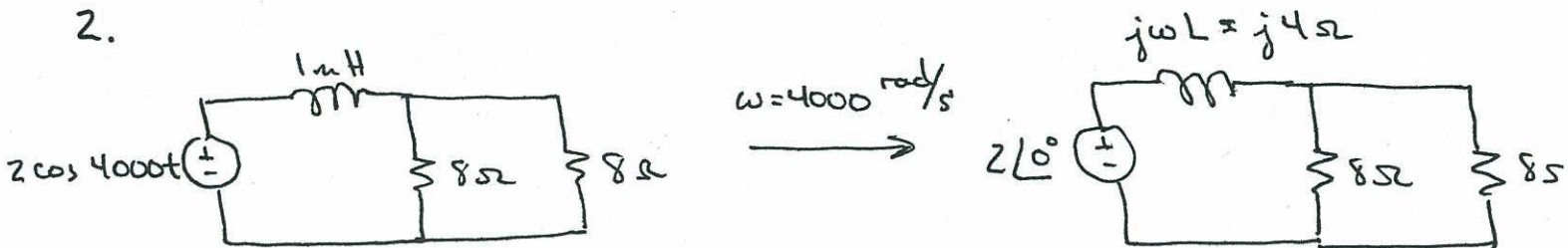

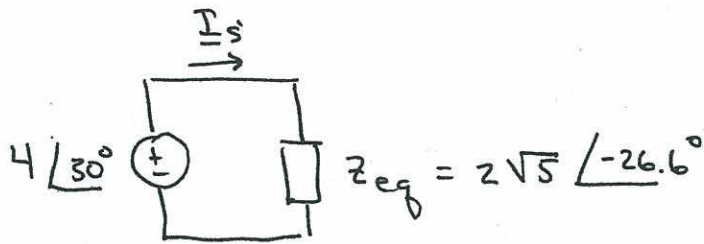
3. From exercise 1, the equivalent circuit is



$$\underline{I}_s = \frac{4\angle 30^\circ}{2\sqrt{5}\angle -26.6^\circ} = \frac{2}{\sqrt{5}}\angle 56.6^\circ$$

$$\underline{i}_s(t) = \frac{2}{\sqrt{5}} \cos(t + 56.6^\circ)$$

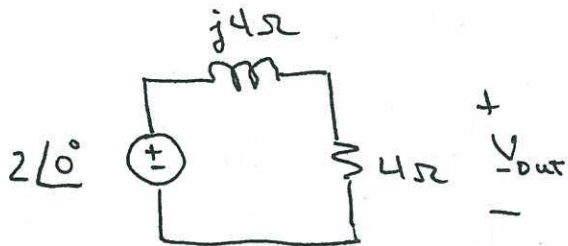4. From exercise 2, the equivalent circuit is:



$$\underline{V}_{out} = 2\angle 0^\circ \left[\frac{4\Omega}{(4+j4)\Omega} \right] = 2\angle 0^\circ \left[\frac{4}{4\sqrt{2}\angle 45^\circ} \right] = \frac{8}{4\sqrt{2}}\angle -45^\circ$$


$$\underline{V}_{out} = \sqrt{2}\angle -45^\circ$$

$$\underline{v}_{out}(t) = \sqrt{2} \cos(4000t - 45^\circ)$$

Exercises
Chapter 10.6

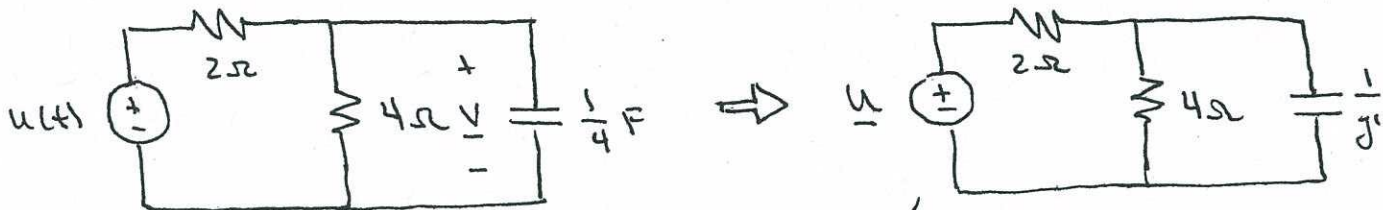1. $u(t) = 4 \cos(t + 30^\circ) + 2 \cos(2t - 45^\circ)$

\uparrow \uparrow
 $\omega = 1$ $\omega = 2$



circuit reduction

$$\frac{4 \cdot \frac{1}{j\omega C}}{4 + \frac{1}{j\omega C}} = \frac{4}{4j\omega C + 1} = \frac{4}{j4\omega(\frac{1}{4}) + 1} = \frac{4}{j\omega + 1}$$

Voltage divider:

$$\underline{v} = \underline{u} \frac{\frac{4}{j\omega + 1}}{2 + \frac{4}{j\omega + 1}} = \frac{4}{6 + j2\omega} \underline{u}$$

$$\omega = 1 \text{ rad/sec} \Rightarrow \underline{v} = \frac{4}{6 + j2(1)} [4 \angle 30^\circ] = (0.63 \angle -18.4^\circ) (4 \angle 30^\circ)$$

$$\underline{v} = 2.52 \angle 11.6^\circ$$

$$\omega = 2 \text{ rad/sec} \Rightarrow \underline{v} = \frac{4}{6 + j2(2)} [2 \angle -45^\circ] = 1.1 \angle -78.7^\circ$$


Superimpose in time domain:

$$\underline{\underline{v(t) = 2.52 \cos(t + 11.6^\circ) + 1.1 \cos(2t - 78.7^\circ)}}$$

Exercises
Chapter 10.6

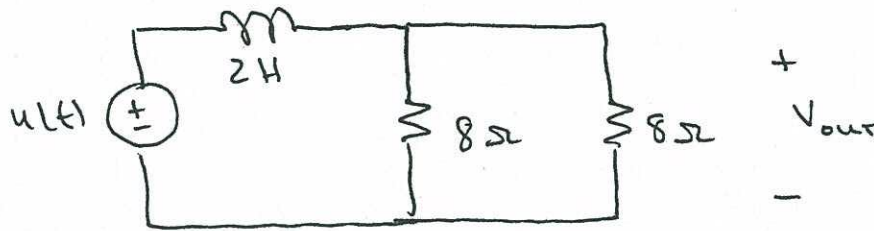2. Total applied voltage:

$$u(t) = u_1(t) + u_2(t) = 4 \cos(2t) + \cos(4t)$$



Circuit reduction & conversion to frequency domain



$$\underline{V}_{out} = \frac{4}{4 + j2\omega} \cdot \underline{u} \quad \leftarrow \text{Voltage divider}$$

$$\omega = 2 \text{ rad/sec} \Rightarrow \underline{V}_{out} = \frac{4}{4 + j4} (4 \angle 0^\circ) = 2\sqrt{2} \angle -45^\circ$$

$$\omega = 4 \text{ rad/sec} \Rightarrow \underline{V}_{out} = \frac{4}{4 + j8} (1 \angle 0^\circ) = 0.45 \angle -63.4^\circ$$

Superimpose in time domain to get total response:

$$\underline{\underline{V_{out}(t) = 2\sqrt{2} \cos(2t - 45^\circ) + 0.45 \cos(4t - 63.4^\circ)}}$$