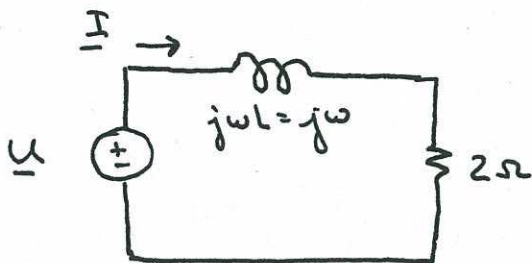


Exercises  
chapter 11.1

1. Frequency domain model:



$$\underline{I} = \frac{\underline{u}}{2 + j\omega} \Rightarrow \underline{\frac{I}{u}} = \underline{\frac{1}{2 + j\omega}}$$

2.  $u(t) = 3 \cos(2t - 60^\circ) + 4 \cos(4t + 30^\circ) + 7 \cos(6t + 45^\circ)$

•  $\omega = 2 \text{ rad/s} \Rightarrow \underline{u}_1 = 3 \angle -60^\circ, |H(j2)| = 0, \angle H(j2) = 0^\circ$

$$\underline{y}_1 = \underline{u}_1 (0 \angle 0^\circ) = 0 \angle -60^\circ$$

•  $\omega = 4 \text{ rad/s} \Rightarrow \underline{u}_2 = 4 \angle 30^\circ, |H(j4)| = 1, \angle H(j4) = 0^\circ$

$$\underline{y}_2 = \underline{u}_2 (1 \angle 0^\circ) = 4 \angle 30^\circ$$

•  $\omega = 6 \text{ rad/s} \Rightarrow \underline{u}_3 = 7 \angle 45^\circ, |H(j6)| = 0, \angle H(j6) = 0^\circ$

$$\underline{y}_3 = \underline{u}_3 (0 \angle 0^\circ) = 0 \angle 45^\circ$$

Superimpose  $\underline{y}_1, \underline{y}_2, \underline{y}_3$  to get  $y(t)$ :


$$y(t) = 0 \cos(2t - 60^\circ) + 4 \cos(4t + 30^\circ) + 0 \cos(6t + 45^\circ)$$

$$\underline{y(t) = 4 \cos(4t + 30^\circ)}$$




Exercises  
Chapter 11.2

1.

(a)


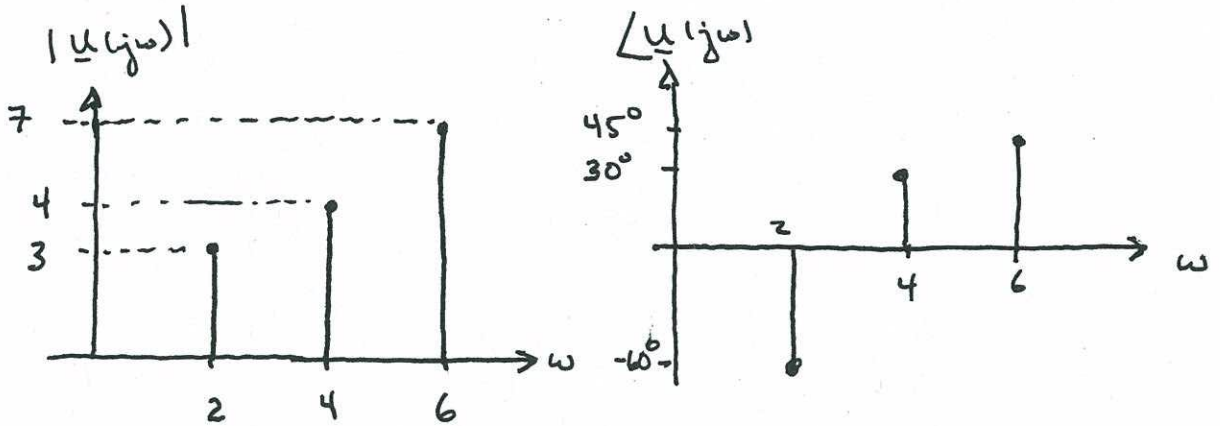


(b)

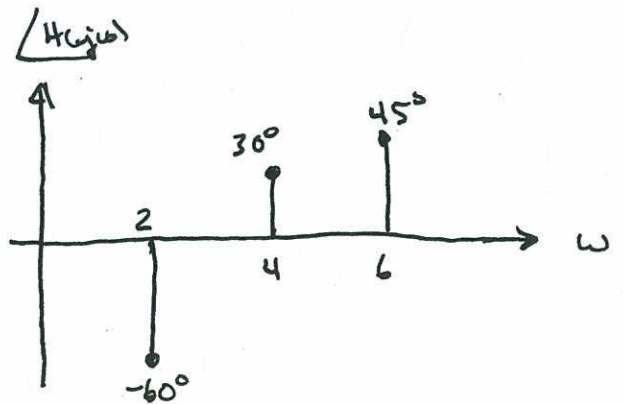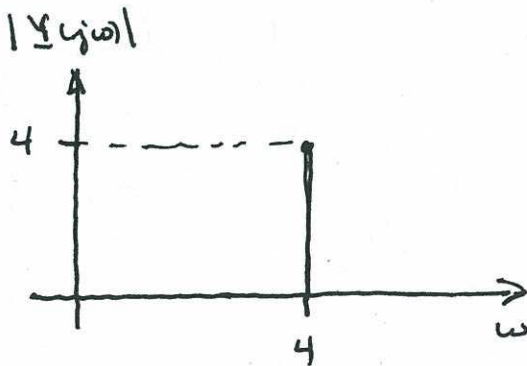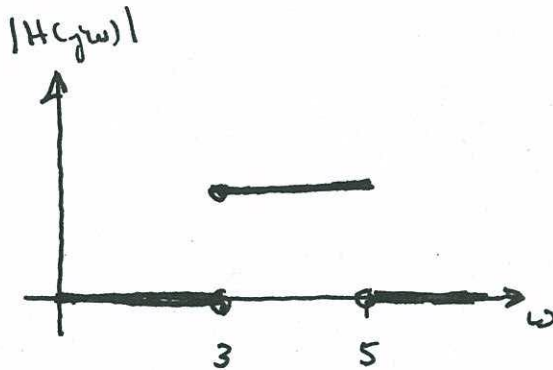


Exercises  
Chapter 11.2

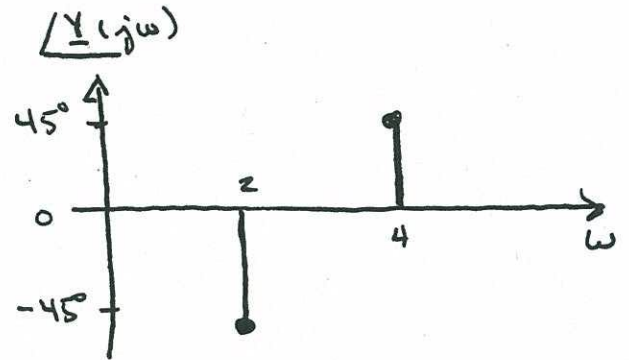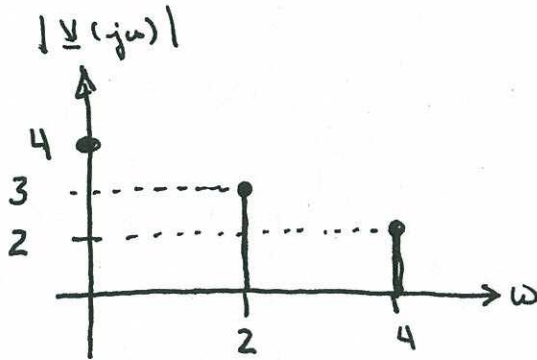2.  $v(t) = 4 + 3 \cos(2t - 45^\circ) + 2 \cos(4t + 45^\circ)$




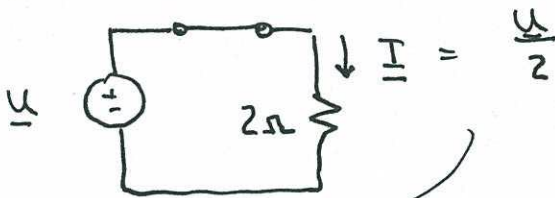3.

$\omega \rightarrow 0$ , inductor shorts:



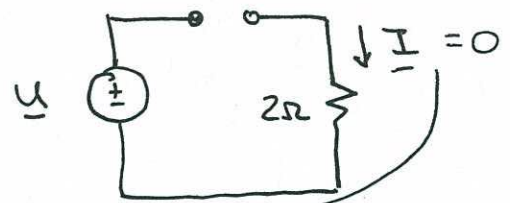$\omega \rightarrow \infty$ , inductor opens



$H(j\omega) = \frac{1}{2}$

$H(j\omega) = 0$

Both check ✓

4.

$\omega \rightarrow 0$ :



$Y = \frac{U}{\infty}$


$\omega \rightarrow \infty$ :



$Y = 0$

Exercises  
Chapter 11.3

1. Frequency domain circuit:

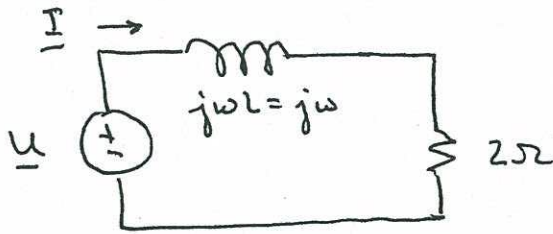

$$\underline{I} = \frac{\underline{u}}{2 + j\omega} \Rightarrow \underline{\frac{I}{u}} = \frac{1}{2 + j\omega}$$



$$\Rightarrow \begin{cases} \left| \frac{I}{u} \right| = \frac{1}{\sqrt{2^2 + \omega^2}} \\ \angle \frac{I}{u} = -\tan^{-1}\left(\frac{\omega}{2}\right) \end{cases}$$

$$\left| \frac{I}{u} \right|_{\max} = \frac{1}{2} \quad (\text{when } \omega = 0)$$


$$\underline{\omega_c = 2 \text{ rad/sec}} \Rightarrow \left| \frac{I}{u} \right|_{\omega = \omega_c} = \frac{1}{\sqrt{2^2 + 2^2}} = \frac{1}{\sqrt{8}} = \frac{1}{\sqrt{2}} \cdot \frac{1}{2}$$

$\frac{1}{\sqrt{2}}$  times maximum value.


2.

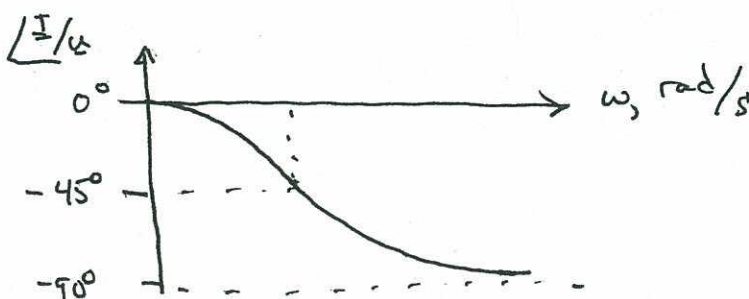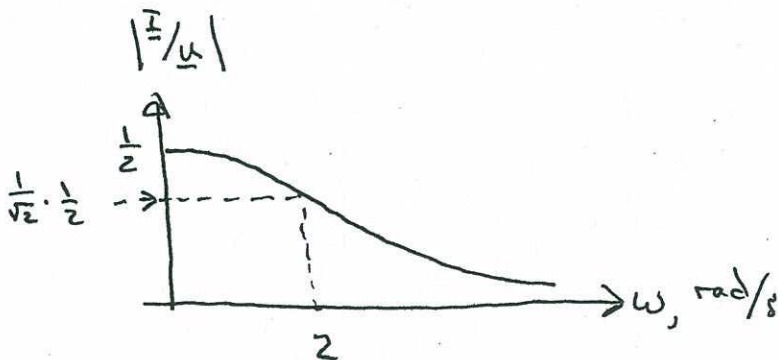

3. Frequency domain circuit:

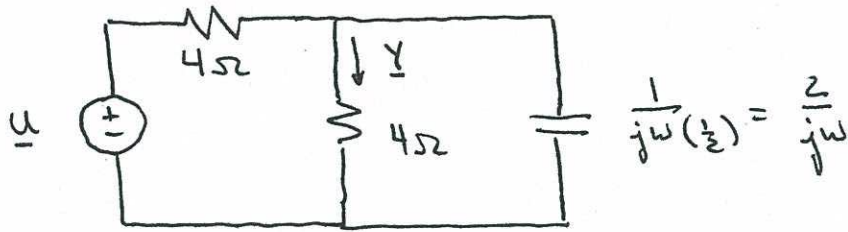

Equivalent circuit:

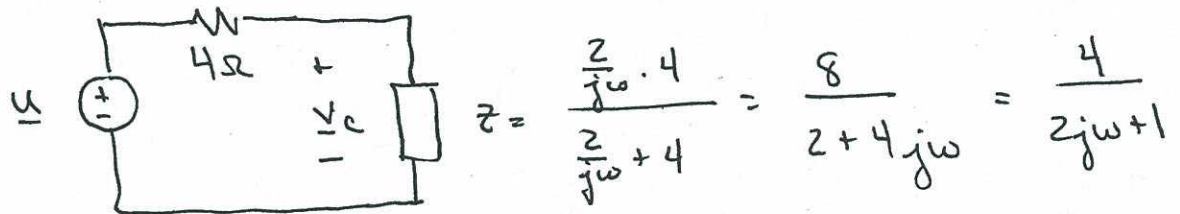

$\underline{v}_c$  from voltage divider:  $\underline{v}_c = \underline{u} \left[ \frac{\frac{4}{2j\omega + 1}}{4 + \frac{4}{2j\omega + 1}} \right]$

$$\underline{v}_c = \underline{u} \frac{4}{8 + j8\omega} = \frac{1}{2 + j2\omega} \underline{u}$$

$$\underline{y} = \frac{\underline{v}_c}{4\Omega} \Rightarrow \underline{y} = \frac{1}{8 + j8\omega} \underline{u} \Rightarrow \underline{\frac{y}{u}} = \frac{1}{8 + j8\omega}$$

$\underline{\omega_c = 1 \text{ rad/s}}$


Time constant:

$R_{eq} = 2\Omega$


$\tau = R_{eq} C = (2\Omega) \left(\frac{1}{2} F\right) = \underline{1 \text{ sec}}$

$\omega_c = \frac{1}{\tau}$

$\omega = 0$ :

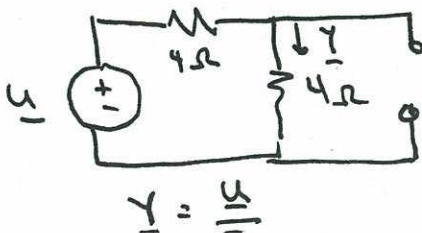

$\omega \rightarrow \infty$ :

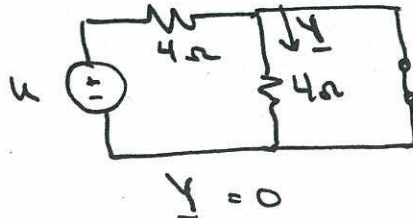



Low pass  
Filter.

Exercises  
Chapter 11.4

1.

$$\frac{Y}{u} = \frac{1}{1+j2\omega}$$

$$\Rightarrow \begin{cases} \text{DC gain} = 1 = 0 \text{ dB} \\ \omega_c = \frac{1}{2} \text{ rad/s} \\ \left| \frac{Y}{u} \right| \rightarrow 0 \text{ as } \omega \rightarrow \infty \end{cases}$$

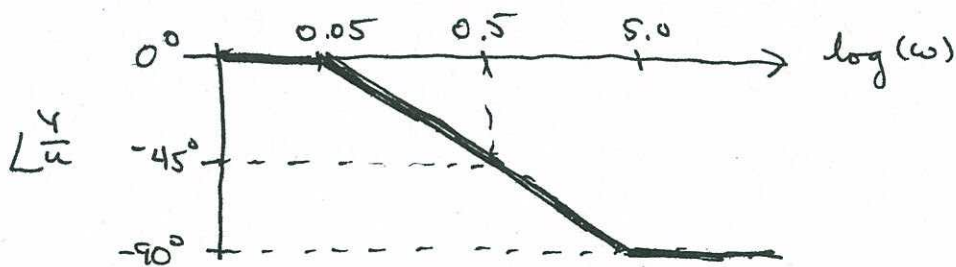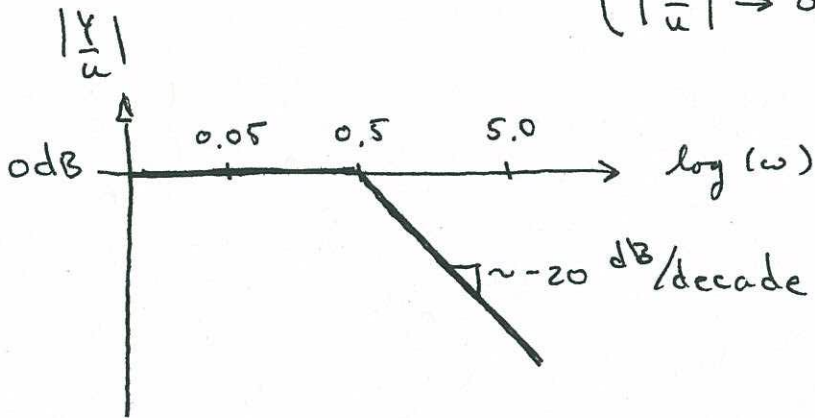



Exercises  
Chapter 11.4

2.

$$\frac{Y}{U} = \frac{1}{8 + j8\omega}$$

$$\Rightarrow \begin{cases} \text{DC gain} = \frac{1}{8} = -18 \text{ dB} \\ \omega_c = 1 \text{ rad/sec} \\ \left| \frac{Y}{U} \right| \rightarrow 0 \text{ as } \omega \rightarrow \infty \end{cases}$$

