

Exercises  
Chapter 12.1

1.  $i(t) = 2 \cos(100t) \Rightarrow \underline{I} = 2 \angle 0^\circ$

$$v(t) = 120 \cos(100t + 65^\circ) \Rightarrow \underline{V} = 120 \angle 65^\circ$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{(120)(2)}{2} \cos(65^\circ - 0^\circ)$$

$$= \underline{\underline{50.7 \text{ W}}}$$

Exercises  
Chapter 12.2

1.  $i(t) = 2 \cos(100t)$

$$v(t) = 120 \cos(100t + 65^\circ)$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{(120)(2)}{2} \cos(65^\circ - 0^\circ)$$

$$\underline{\underline{P = 50.7 \text{ W}}}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{(120)(2)}{2} \sin(65^\circ - 0^\circ)$$

$$\underline{\underline{Q = 108.76 \text{ VAR}}}$$

Exercises

Chapter 12.3

1.  $i(t) = 2 \cos(100t)$

$$\underline{\underline{I_{RMS} = \frac{2}{\sqrt{2}}}}$$

$$v(t) = 120 \cos(100t + 65^\circ)$$

$$\underline{\underline{V_{RMS} = \frac{120}{\sqrt{2}}}}$$

Exercises  
chapter 12.4

1.  $v(t) = 120 \cos(100t + 65^\circ)$

$$i(t) = 2 \cos(100t)$$

$$\text{Apparent power} = \frac{(120)(2)}{2} = \underline{\underline{120 \text{ VA}}}$$

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(65^\circ - 0^\circ) = \underline{\underline{0.42}}$$


2.  $P = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta_v - \theta_i)$

$$100,000 \text{ W} = V_{\text{RMS}} (256 \text{ A}) (0.85)$$


$$V_{\text{RMS}} = \frac{100,000 \text{ W}}{(256 \text{ A})(0.85)} = \underline{\underline{460 \text{ V}}}$$

3.  $\theta = \cos^{-1}(0.9) = \underline{\underline{25.8^\circ}}$

Exercises  
Chapter 12.5

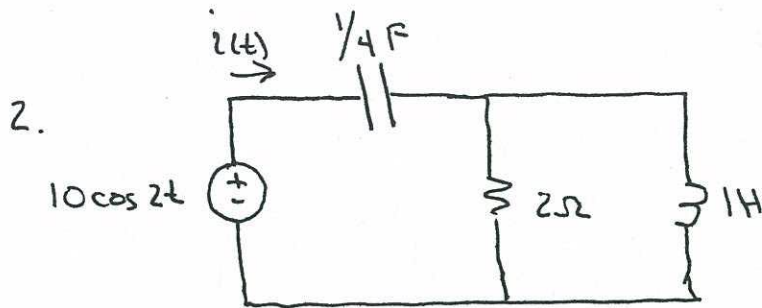

Impedance domain circuit

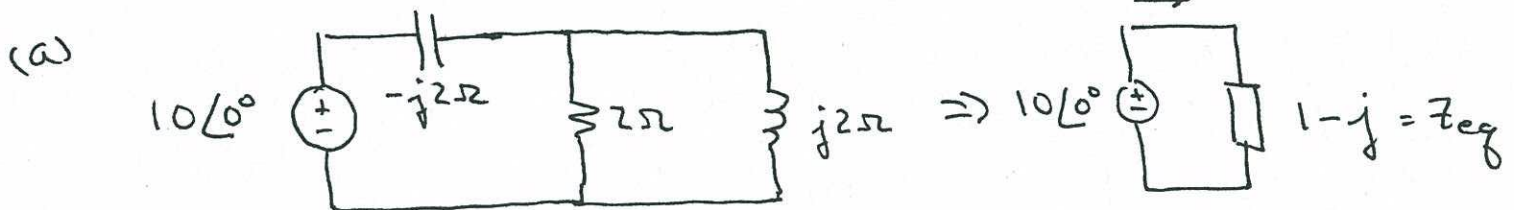

$$\underline{I} = \frac{10\angle 0^\circ}{1-j} = \frac{10\angle 0^\circ}{\sqrt{2}\angle -45^\circ} = \frac{10}{\sqrt{2}}\angle 45^\circ$$

$$\underline{i(t)} = \frac{10}{\sqrt{2}} \cos(2t + 45^\circ)$$

(b)

$$S = \frac{VI^*}{2} = \frac{(10\angle 0^\circ)(\frac{10}{\sqrt{2}}\angle -45^\circ)}{2}$$

$$S = \frac{50}{\sqrt{2}}\angle -45^\circ \text{ VA}$$

Note: complex conjugate change sign on phase angle

(c)

$$P = \frac{VI}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{(10)(\frac{10}{\sqrt{2}})}{2} \cos(-45^\circ)$$

$$P = 25 \text{ W}$$