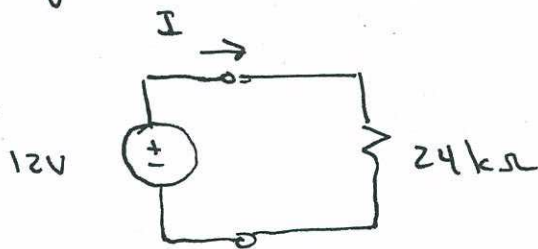


Exercises  
Chapter 2.1

1. Resistors are in series, so the equivalent resistance is:

$$R_{eq} = 10k\Omega + 4k\Omega + 4k\Omega + 6k\Omega \\ = 24k\Omega$$

Equivalent circuit:



$$I = \frac{12V}{24k\Omega} = 0.5A$$

All elements have same current, so:

$$V_1 = (4k\Omega)(0.5A) = \underline{\underline{2V}}$$

ALTERNATE: Voltage divider

$$V_1 = 12V \left( \frac{4k\Omega}{10k\Omega + 4k\Omega + 4k\Omega + 6k\Omega} \right) = 12V \left( \frac{4k\Omega}{24k\Omega} \right)$$

$$\underline{\underline{V_1 = 2V}}$$

## Exercises

## chapter 2.2

1. Easiest approach is probably a current divider:

$$I = 5 \text{ mA} \left( \frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 5 \text{ k}\Omega} \right) = 5 \text{ mA} \left( \frac{3}{8} \right)$$

$$\underline{\underline{I = \frac{15}{8} \text{ mA}}}$$


2. Probably easiest to use current divider formula:

$$I = 3 \text{ mA} \left( \frac{R}{R + 1 \text{ k}\Omega} \right) = 2 \text{ mA}$$

$$\frac{R}{R + 1 \text{ k}\Omega} = \frac{2}{3} \quad \Rightarrow \quad \underline{\underline{R = 2 \text{ k}\Omega}}$$

Exercises  
Chapter 2.3


1(a)

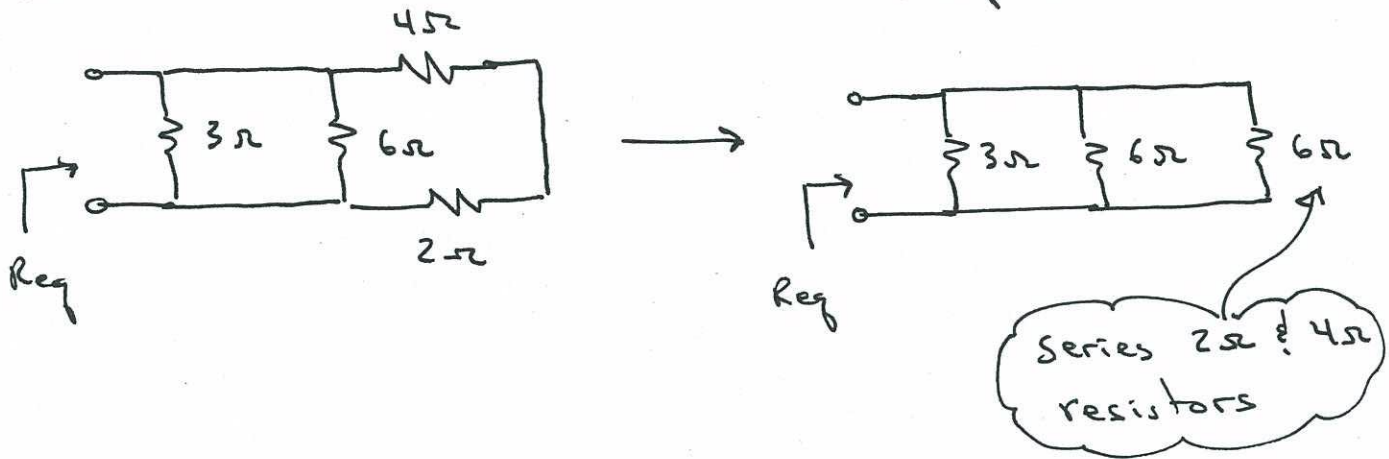

Combine parallel 3Ω, 6Ω, 6Ω resistors:

$$R_{eq} = \frac{1}{\frac{1}{3\Omega} + \frac{1}{6\Omega} + \frac{1}{6\Omega}} = \underline{\underline{1.5\Omega}}$$

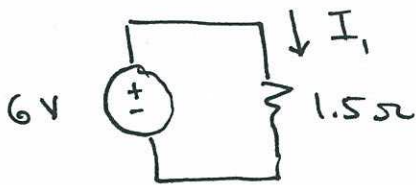(b) From the above, an equivalent circuit is:




$$I_1 = \frac{6V}{1.5\Omega} = \underline{\underline{4A}}$$

could use current divider &  $I_1$ , above to get  $I_2$ , but probably easier to use Ohm's law:


$$I_2 = \frac{6V}{3\Omega} \Rightarrow \underline{\underline{I_2 = 2A}}$$

Exercises  
Chapter 2.4

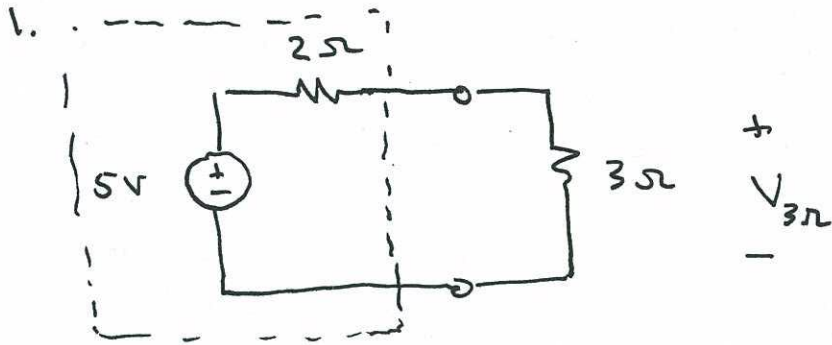

voltage divider:
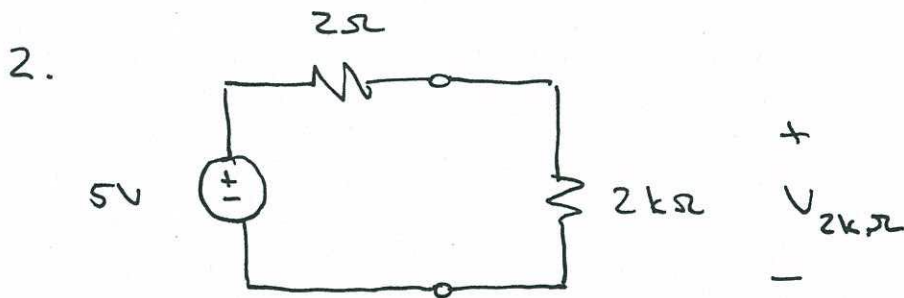
$$V_{3\Omega} = 5V \left( \frac{3\Omega}{2\Omega + 3\Omega} \right) = \underline{\underline{3V}}$$




voltage divider:

$$V_{2k\Omega} = 5V \left( \frac{2000\Omega}{2000\Omega + 2\Omega} \right) = \underline{\underline{4.995V}}$$

Exercises

chapter 2.5

1.

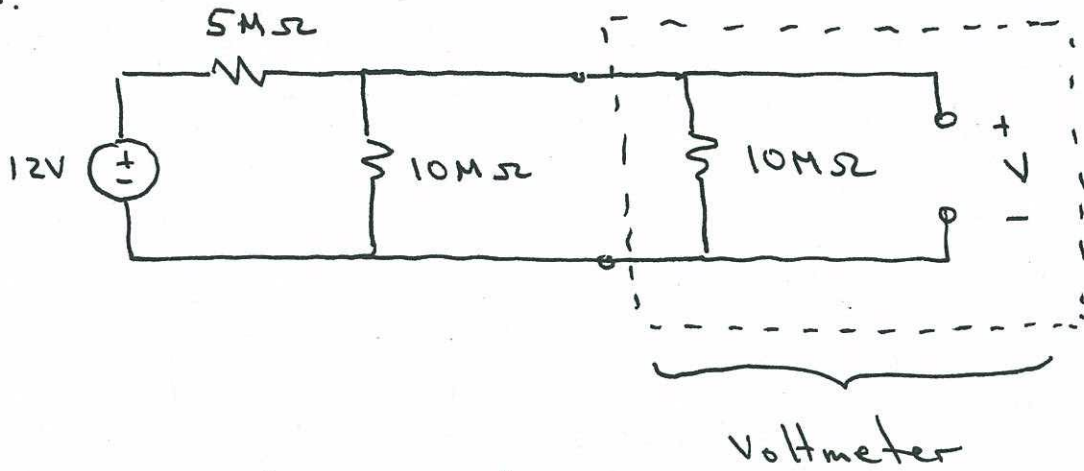

Equivalent circuit



$$V = \left( \frac{5M\Omega}{5M\Omega + 5M\Omega} \right) 12V \Rightarrow \underline{\underline{V = 6V}}$$