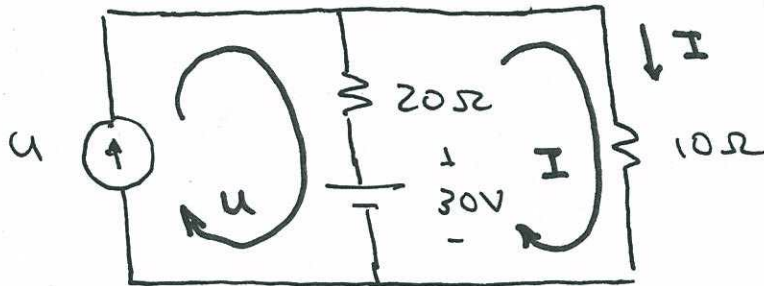


Exercises
chapter 4.1

1. Rather arbitrarily, use mesh analysis.
Mesh & dependent loops shown below:




$$\text{KVL, Loop I: } -30\text{V} + 20\Omega (I - u) + 10\Omega (I) = 0$$

$$30 + 20u = 30I$$

$$\underline{\underline{I = 1 + \frac{2}{3}u}}$$

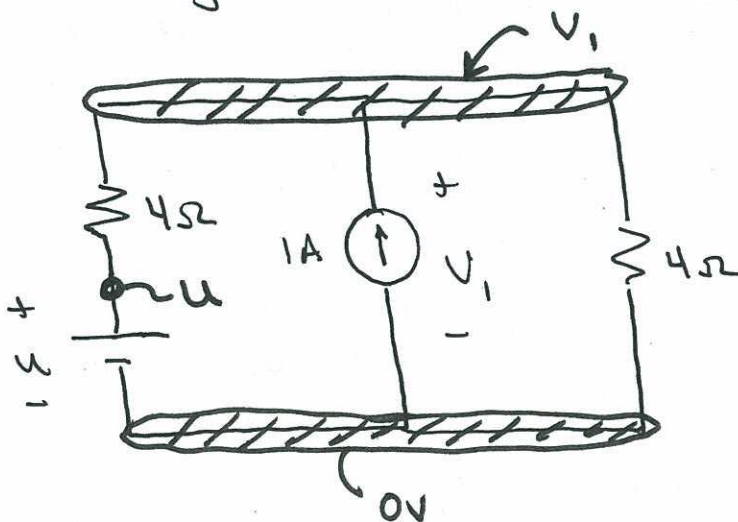2. Use nodal analysis. Node voltages & dependent voltages shown below:



KCL, node V_1 :

$$\frac{V_1 - u}{4\Omega} - 1\text{A} + \frac{V_1}{4\Omega} = 0$$

$$2V_1 = u + 4$$

$$\underline{\underline{V_1 = \frac{u + 4}{2}}}$$

Exercises
Chapter 4.2

1.


$$(a) \quad V_a = 20\Omega (2A) = 40V$$

$$(b) \quad V_b = 20\Omega (3A) = 60V$$


$$(c) \quad V_c = 20\Omega (5A) = 100V$$

$V_c = V_a + V_b \Rightarrow$ looks like superposition holds!

2.

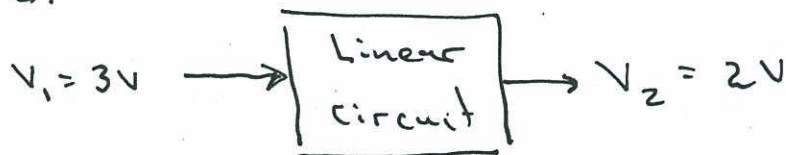

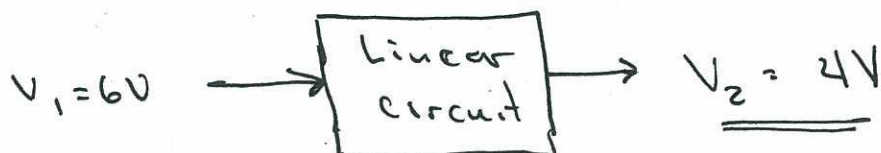\downarrow multiply input by 2, so output
also scaled by 2




Exercises


Chapter 4.3

1.

(a) Contribution from 8V source:

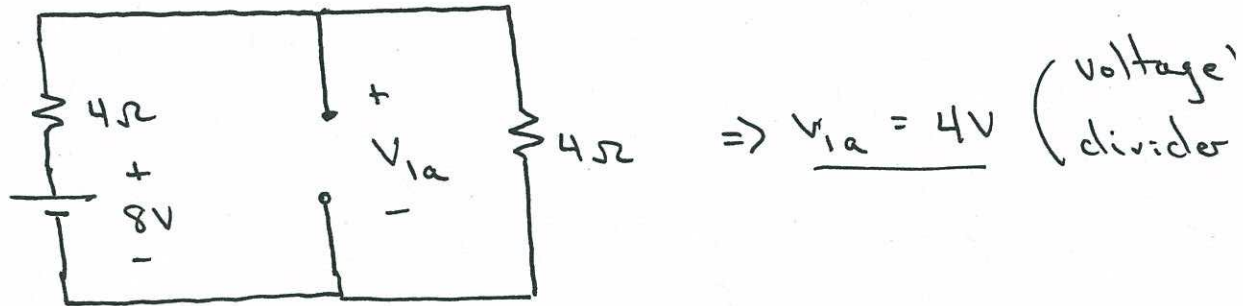


(b) Contribution from 1A source:

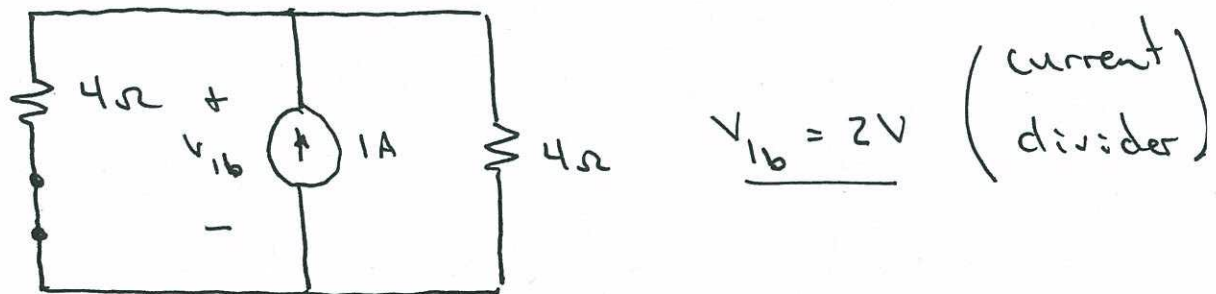

$$V_1 = V_{1a} + V_{1b} = 4V + 2V$$

$$\underline{\underline{V_1 = 6V}}$$

Exercises
Chapter 4.4

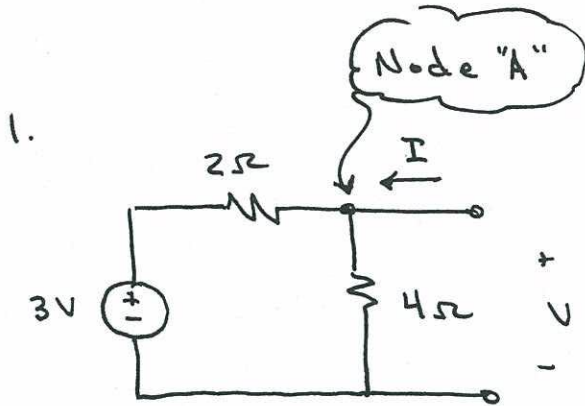


$$\text{KCL at A: } I = \frac{V}{4\Omega} + \frac{V - 3V}{2\Omega}$$

$$\underline{\underline{4I = 3V - 6}} \quad \leftarrow \text{(or any other equivalent mathematical statement)}$$


Exercises
Chapter 4.5

1. Find R_{Th} :

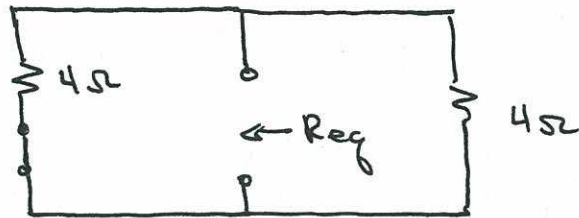


$$R_{eq} = 2\Omega$$

Find V_{oc} :

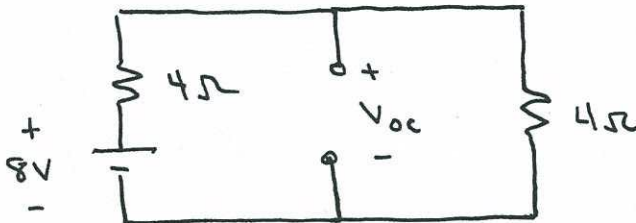


$$V_{oc} = 4V$$

Thevenin circuit:

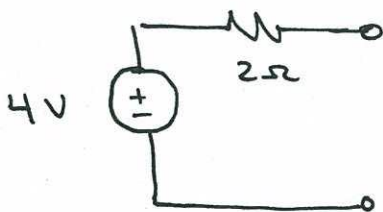

To find V_1 :

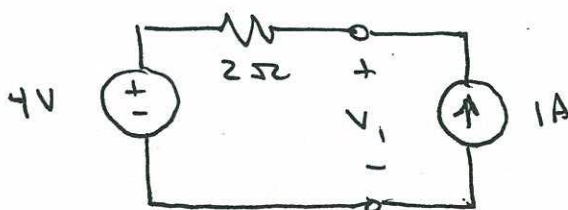


$$V_1 = 4V + 2\Omega(1A)$$

$$\underline{\underline{V_1 = 6V}}$$


Exercises
Chapter 4.5

2. Find R_{TH} :

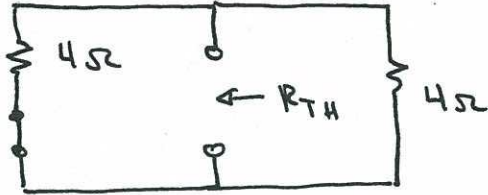


$$R_{TH} = 2\Omega$$

Find I_{sc}

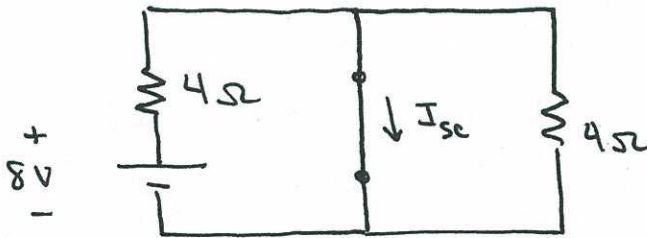


$$I_{sc} = 2A$$

Norton circuit:

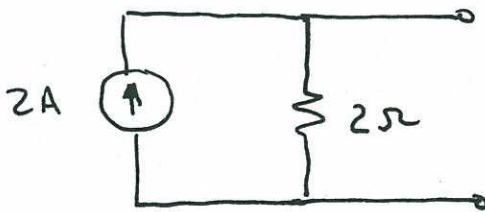

Find V_1 :

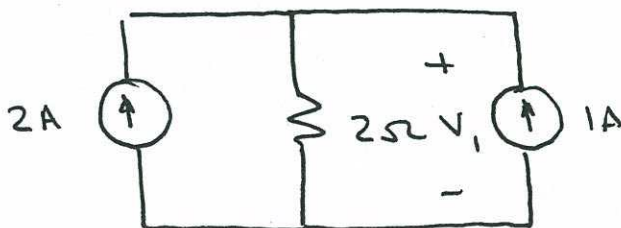

$$V_1 = (3A)(2\Omega)$$

$$\underline{\underline{V_1 = 6V}}$$


Exercises
Chapter 4.5

3.

We are given (basically) a
Thevenin circuit. To convert to a

Norton circuit, $I_{sc} = \frac{V_{oc}}{R_{TH}} = \frac{12V}{4\Omega} = 3A$

The Norton circuit is:

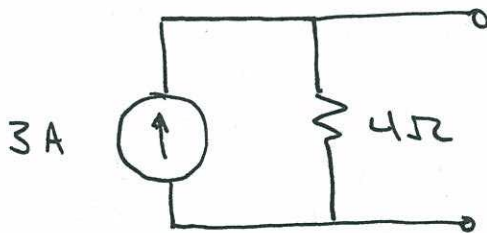

Exercises
Chapter 4.6

1. The circuit to the left of the resistor R is a Thevenin circuit. Therefore, for maximum power, set:

$$R = R_{TH} = \underline{\underline{24\Omega}}$$