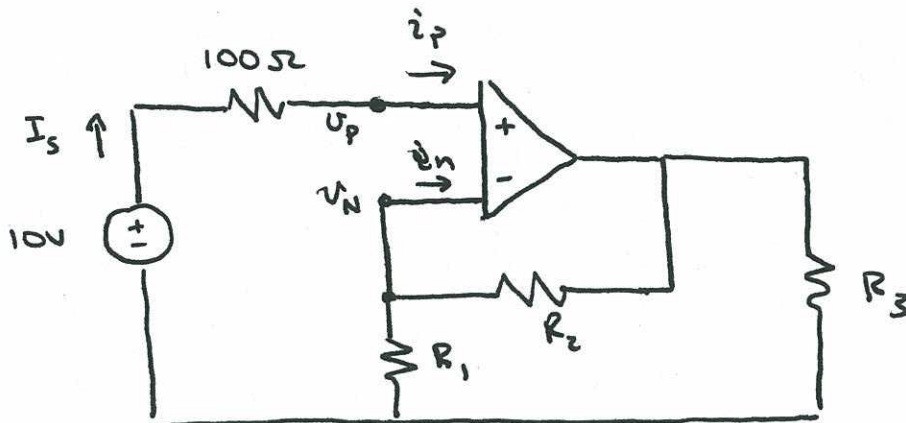


Exercises
chapter 5.1

1.



Op-amp rules for the above circuit:

(1) $v_p = v_n$

(2) $i_p = i_n = 0$

(a) Since $i_p = 0 \Rightarrow \underline{I_s = 0}$ (they are in series)

(b) Since $i_s = 0 \Rightarrow$ there is no current through the $100\ \Omega$ resistor $\hat{=}$ no voltage drop across the $100\ \Omega$ resistor $\Rightarrow \underline{v_p = 10V}$

(c) Since $v_p = v_n$, and from (b):

$$\underline{v_n = 10V}$$

Exercises

Chapter 5.2

$$K = 10,000$$

$$V^+ = 20V$$

$$V^- = -10V$$

For an op-amp, $V_{out} = K(v_p - v_n)$ but

$$V^- < V_{out} < V^+$$

$$(a) \quad v_p - v_n = 1mV \Rightarrow V_{out} = 10,000(.001) = \underline{\underline{10V}}$$

$$(b) \quad v_p - v_n = 2mV \Rightarrow V_{out} = 10,000(.002) = \underline{\underline{20V}}$$

$$(c) \quad v_p - v_n = 4mV \Rightarrow V_{out} = 10,000(.004) = 40V$$

$$\underline{\underline{BUT}} \quad V_{out} < V^+ \Rightarrow \underline{\underline{V_{out} = 20V}}$$

$$(d) \quad v_p - v_n = -0.2mV \Rightarrow V_{out} = 10,000(-0.0002) = \underline{\underline{-2V}}$$

$$(e) \quad v_p - v_n = -2mV \Rightarrow V_{out} = 10,000(-0.002) = -20V$$


$$\underline{\underline{BUT}} \quad V^- < V_{out} \Rightarrow \underline{\underline{V_{out} = -10V}}$$

Exercises
Chapter 5.4


1. The circuit of Example 2 is governed by the relation:

$$V_{out} = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$


As a VCVS:

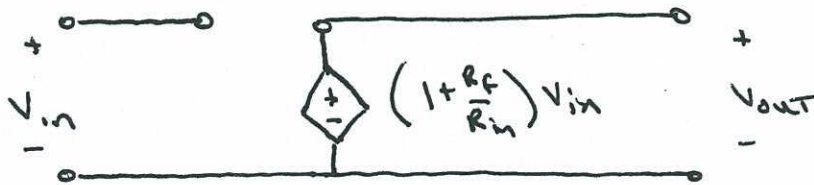

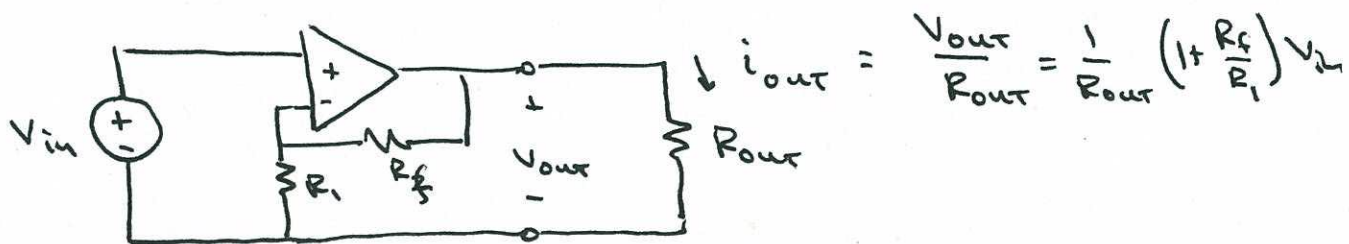2. Since the circuit of Example 2 sets a voltage we need to have an output resistance to find the current. The circuit becomes:




As a voltage controlled current source:

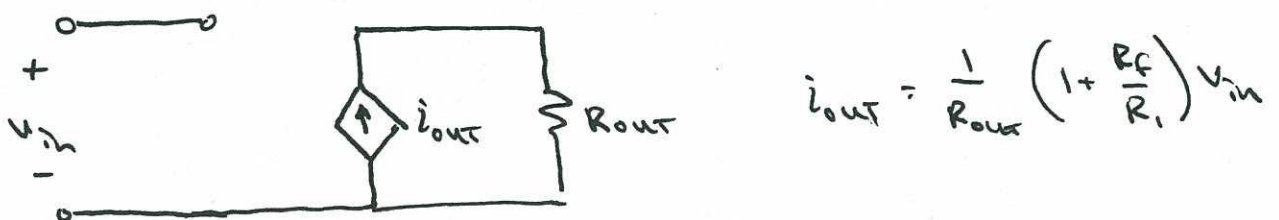

Exercises
chapter 5.4

3.

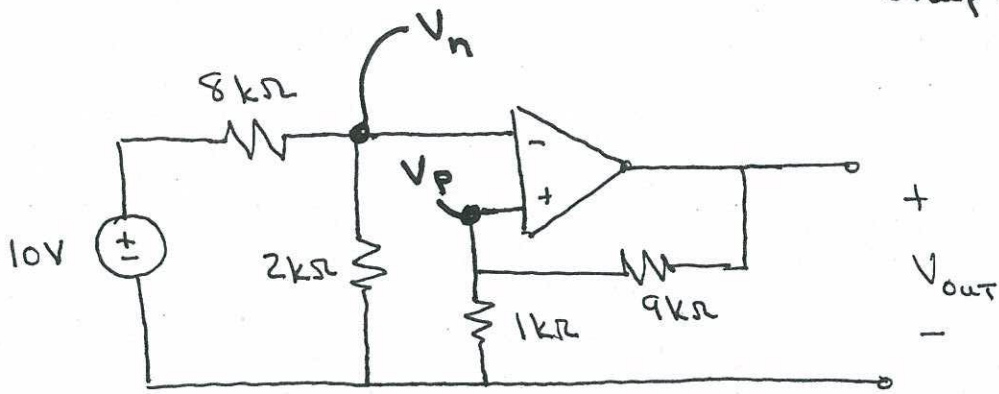


$$V_n = 10V \left[\frac{2k\Omega}{2k\Omega + 8k\Omega} \right] = 2V \quad (\text{voltage divider})$$

$$V_p = V_n = 2V \quad (\text{op-amp rules})$$

$$\text{KCL at non-inverting input: } \frac{2V - 0}{1k\Omega} = \frac{V_{out} - 2V}{9k\Omega}$$

$$\underline{\underline{V_{out} = 20V}}$$

4.

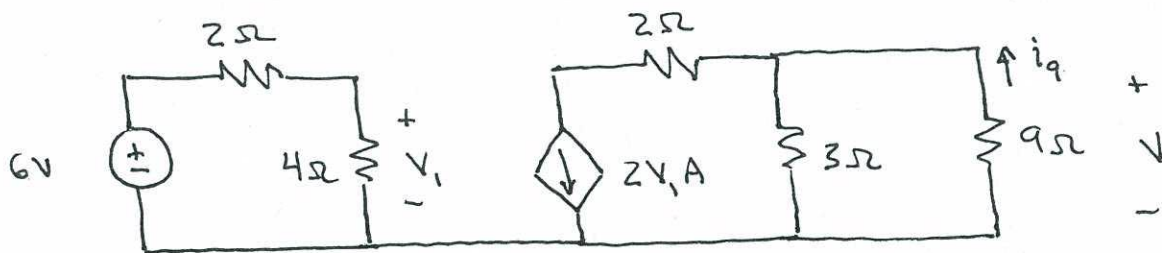


$$V_1 = 6V \left(\frac{4\Omega}{2\Omega + 4\Omega} \right) = 4V \quad (\text{voltage divider})$$

$$2V_1 = 8A \quad (\text{dependent source current})$$

$$i_q = 8A \left[\frac{3\Omega}{3\Omega + 9\Omega} \right] = 2A \quad (\text{voltage divider})$$

$$V = -i_q (9\Omega) \Rightarrow \underline{\underline{V = -18V}}$$

Exercises
Chapter 5.5

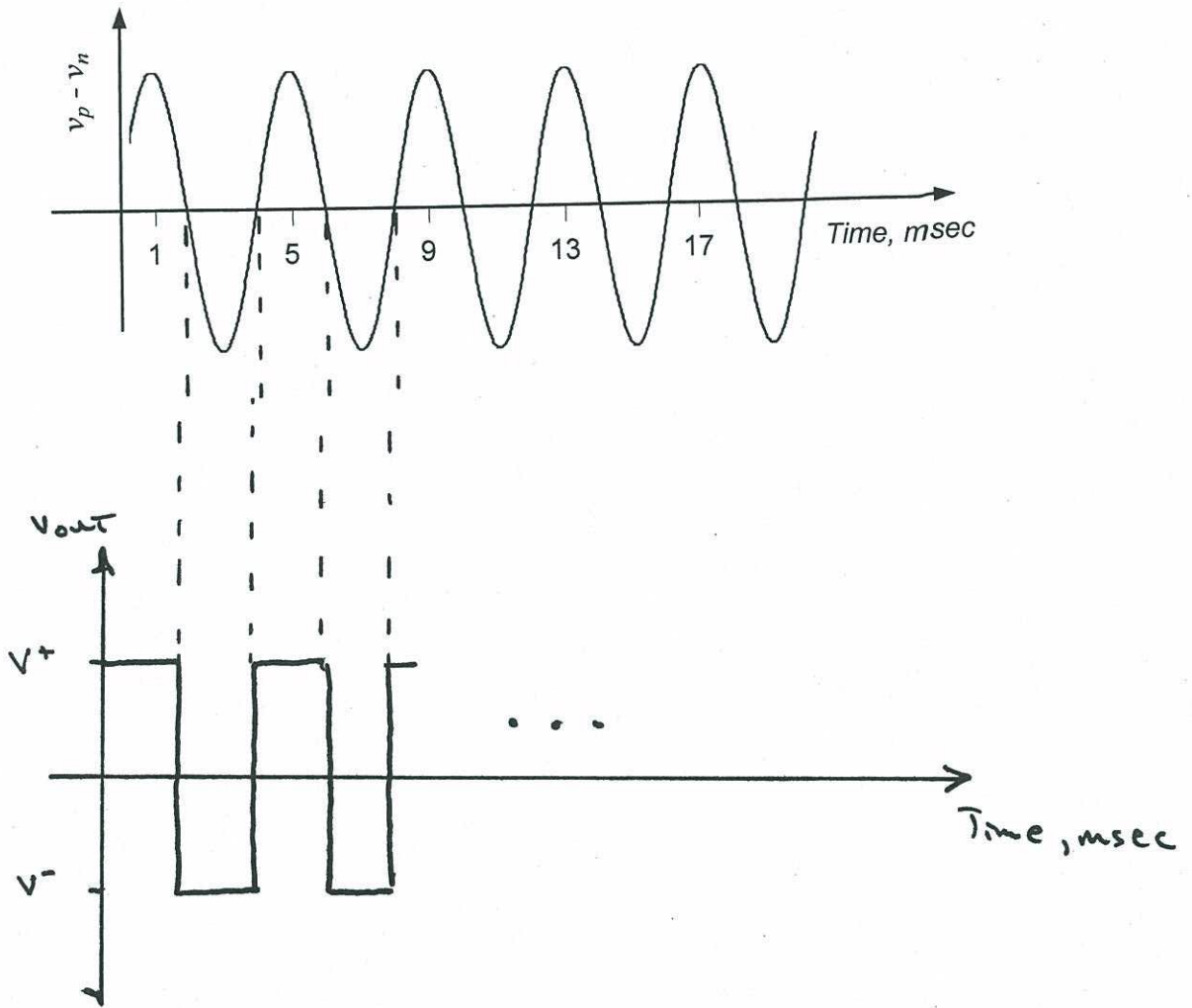

↗
The output voltage is v^+ if
 $v_p - v_n > 0$ and v^- if $v_p - v_n < 0$.