

Exercises
Chapter 7.1

1. (a)

i. Equation is: $mc_p \frac{d(T_B - T_0)}{dt} + h(T_B - T_0) = 0$

as $t \rightarrow \infty$, temperatures become constant,

and $\frac{d(T_B - T_0)}{dt} \rightarrow 0$. Therefore:

$$h(T_B - T_0) = 0 \Rightarrow \underline{T_B = T_0}$$

Body temperature approaches ambient temperature as $t \rightarrow \infty$


ii. To find time constant, write equation in the form $\frac{dy}{dt} + \frac{1}{\tau} y = 0$:

$$\frac{d(T_B - T_0)}{dt} + \frac{h}{mc_p} (T_B - T_0) = 0 \Rightarrow \underline{\underline{\tau = \frac{mc_p}{h}}}$$

iii. If mass doubles, the time constant doubles. Makes sense, since a larger mass should take longer to cool down.

Exercises
Chapter 7.1

1(a) continued

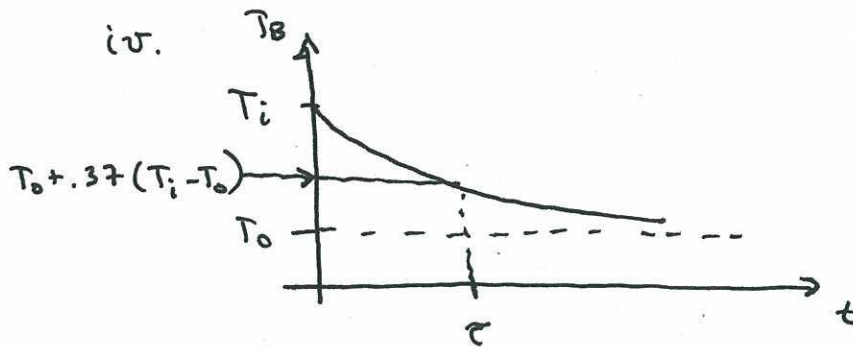

(b)

i) Governing equation: $m c_p \frac{d(T_B - T_0)}{dt} + h(T_B - T_0) = q_{in}$

The input is constant, so all temperatures become constant as $t \rightarrow \infty$ and $\frac{d(T_B - T_0)}{dt} \rightarrow 0$:

$$h(T_B - T_0) = q_{in} \Rightarrow \underline{\underline{T_B = \frac{q_{in}}{h} + T_0}} \text{ as } t \rightarrow \infty$$

ii. Doubling the heat input doubles the increase in body temperature (above T_0).

Reasonable - more heat gives higher temp.

iii. Doubling mass does not affect the final temperature. Mass only affects how quickly the mass can heat up & cool down.

Exercises
chapter 7.1

1(b) - continued

iv. Write equation in form $\frac{dy}{dt} + \frac{1}{\tau} y = f(t)$

$$\frac{d(T_B - T_0)}{dt} + \frac{h}{m c_p} (T_B - T_0) = \frac{q_{in}}{m c_p}$$

$$\tau = \frac{m c_p}{h}$$


doubling mass doubles
time constant, as in
part (a)

v.

$$T_0 + \frac{q_{in}}{h}$$

$$T_0 + 0.63 \frac{q_{in}}{h}$$


T_0

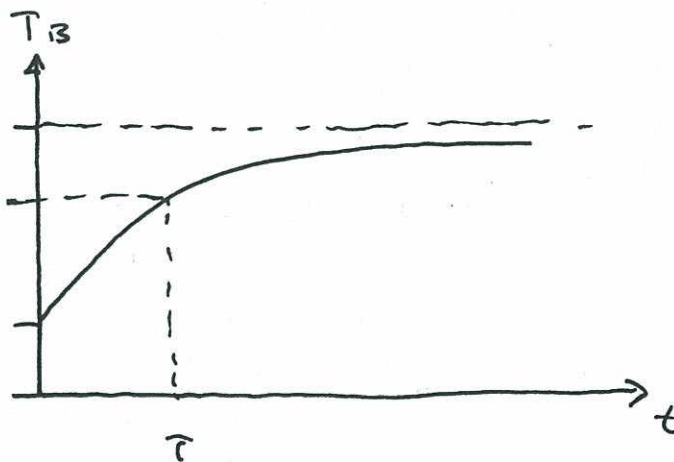

Exercises
Chapter 7.2

1.

(a) circuit for $t > 0$:

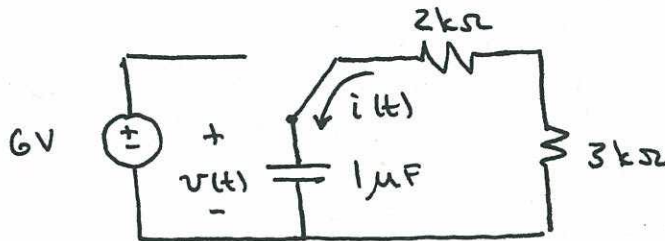

KVL, right loop: $v(t) + (3\text{k}\Omega)i(t) + (2\text{k}\Omega)i(t) = 0$

$$i(t) = C \frac{dv}{dt}$$

$$v(t) + 5\text{k}\Omega \left(1\mu\text{F} \frac{dv}{dt} \right) = 0$$

$$\underline{\underline{\frac{dv(t)}{dt} + 200 v(t) = 0}}$$

(b) $\tau = \frac{1}{200} \text{ sec} = \underline{\underline{0.005 \text{ sec}}}$

(c) Equivalent resistance:



$$R_{eq} = 5\text{k}\Omega$$


$$\tau = R_{eq} C = (5\text{k}\Omega)(1\mu\text{F})$$

$$\underline{\underline{\tau = 0.005 \text{ sec}}}$$

CHECKS!

1. (cont'd)

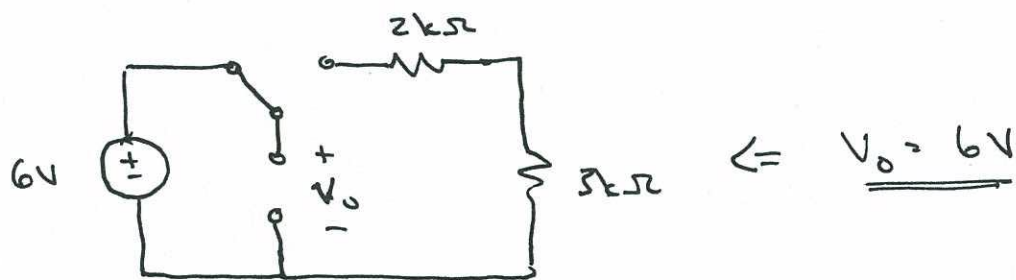(d) For $t < 0$, the switch is in position A and the capacitor looks like an open circuit (constant input, switch has been in position A for a long time) and the circuit looks like:



Voltages across capacitors can't change suddenly, so initial condition is:


$$v(t=0^+) = v(t=0^-) = \underline{6V}$$

(e) Form of solution is $v(t) = V_0 e^{-t/\tau}$, so:

$$\underline{v(t) = 6 e^{-200t} \text{ V}, t > 0}$$

Exercises
Chapter 7.3

1.

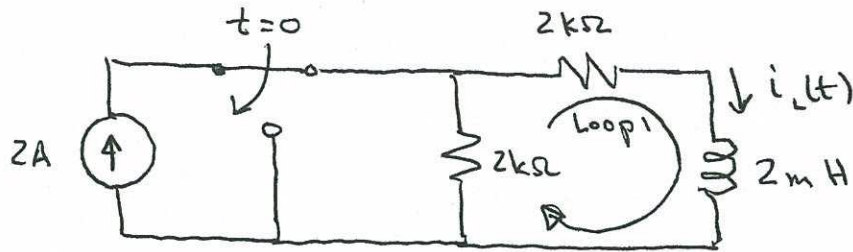

$$+ \frac{di_L}{dt}$$

$$- L$$


(a) KVL, loop 1, $t > 0$:

$$(2k\Omega) i_L + (2k\Omega) i_L + 2mH \frac{di_L}{dt} = 0$$

$$\underline{\underline{\frac{di_L}{dt} + 2 \times 10^6 i_L = 0}}$$

(b) From (a), $\tau = \frac{1}{2} \mu\text{sec}$


(c)

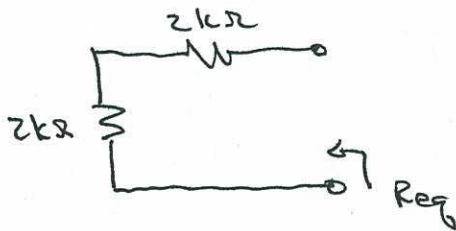

$$\Rightarrow R_{eq} = 2k\Omega + 2k\Omega = 4k\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2mH}{4k\Omega} = \underline{\underline{\frac{1}{2} \mu\text{sec}}}$$

(d) $t = 0^-$:

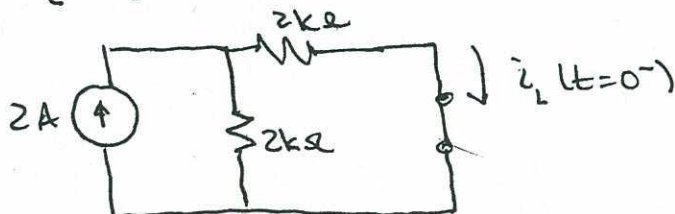

} inductor acts as short circuit at $t=0^-$

$$i_L(t=0^-) = 1A \quad \Leftarrow \text{circuit is a current divider}$$

$$i_L(t=0^+) = i_L(t=0^-) = \underline{\underline{1A}} \quad \Leftarrow \text{inductor current cannot change instantly.}$$


(e) From (a), $\frac{di_L}{dt} + 2 \times 10^6 i_L = 0 \Rightarrow \tau = 0.5$

From (b), $i_L(t=0^+) = 1A = I_0$

Form of solution: $i_L(t) = I_0 e^{-t/\tau}$


$i_L(t) = 1 e^{-2 \times 10^6 t}, t > 0$

(f) $t=0^-$:

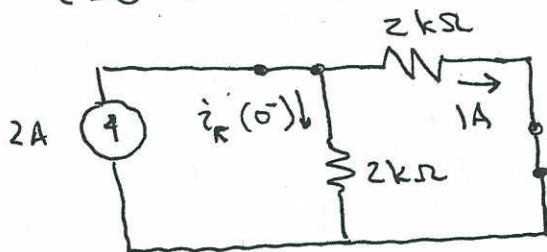

$i_R(t=0^-) = 1A$ (current divider)

$i_L(t=0^-) = 1A$ (current divider)

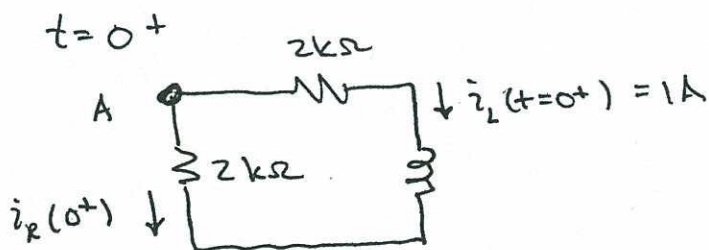


At $t=0^+$, $i_L(t=0^+) = 1A$
(inductor current can't change suddenly)



KCL at A: $i_R(t=0^+) = -$

Resistor current is not continuous with time. (It changes suddenly to compensate for the change in applied current.) The other resistor's current is continuous with time.

Exercises
Chapter 7.4

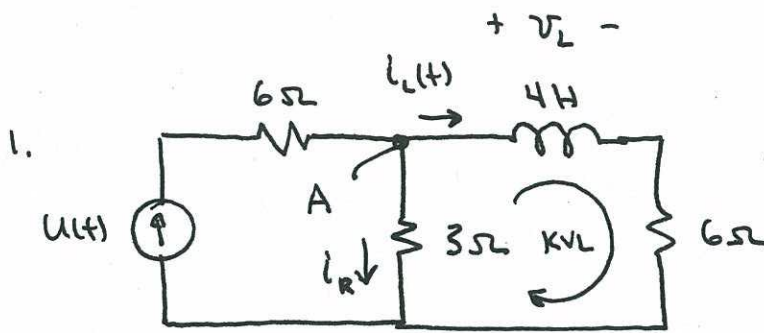

KCL at node A: $i_R = u(t) - i_L(t)$

KVL around right loop:


$$3\Omega (i_R) = v_L + 6\Omega (i_L) \quad ; \quad v_L = 4 \frac{di_L}{dt}$$

$$3\Omega (u - i_L) = 4 \frac{di_L}{dt} + 6\Omega (i_L)$$

$$\underline{\underline{3u = 4 \frac{di_L}{dt} + 9i_L}}$$

Exercises
Chapter 7.4

2.

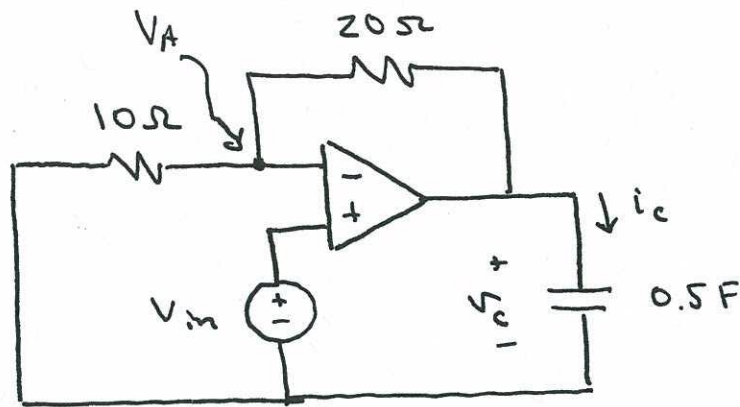

OP-amp rules : $V_A = V_{in}$


KCL at inverting input : $\frac{V_A - 0V}{10\Omega} + \frac{V_A - V_c}{20\Omega} = 0$

$$V_c = 3V_A = 3V_{in}$$

$$i_c = (0.5F) \frac{dV_c}{dt} = 0.5 \left[\frac{d}{dt} (3V_{in}) \right]$$

$$\underline{\underline{i_c(t) = \frac{3}{2} \frac{dV_{in}}{dt}}}$$

Exercises
Chapter 7.4

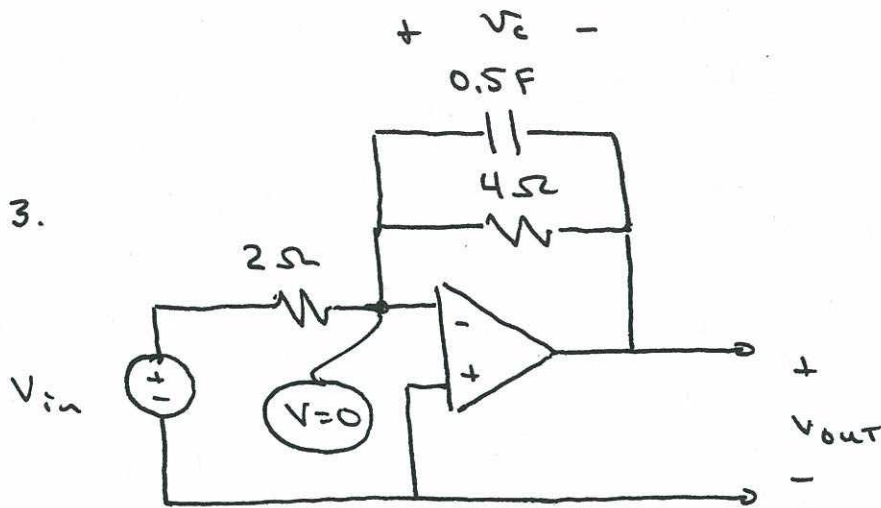

KCL at inverting input:


$$\frac{V_{in} - 0V}{2\Omega} = (0.5F) \frac{dV_c}{dt} + \frac{0 - V_{out}}{4\Omega}$$

$$V_c = -V_{out}$$

$$\frac{V_{in}}{2} = -0.5 \frac{dV_{out}}{dt} - \frac{V_{out}}{4}$$

$$\underline{\underline{2 \frac{dV_{out}}{dt} + V_{out} = -2V_{in}}}$$

Exercises
Chapter 7.5

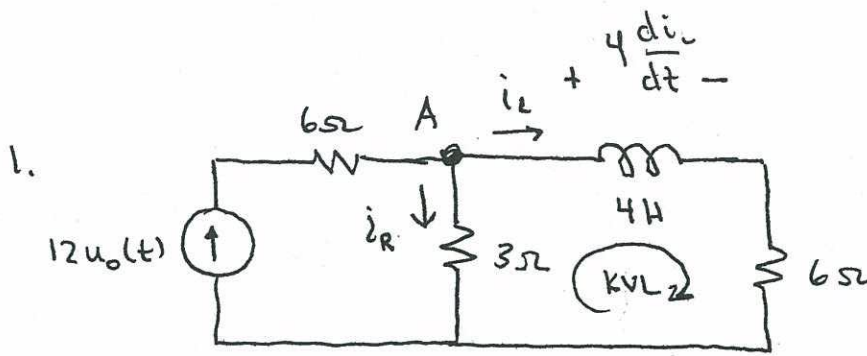

(a) KCL at node A gives: $i_R = 12A - i_L$

KVL around right loop then results in:

$$3\Omega (12A - i_L) = 4 \frac{di_L}{dt} + 6\Omega (i_L)$$

$$36 = 4 \frac{di_L}{dt} + 6i_L$$


$$\underline{\underline{\frac{di_L}{dt} + \frac{9}{4} i_L = 9}}$$

(b) From (a), $\frac{9}{4} = \frac{1}{\tau} \Rightarrow \underline{\underline{\tau = \frac{4}{9} \text{ sec}}}$

(c) $i_L(t) = K_1 + K_2 e^{-t/\tau}$

(d) $t=0^+ \Rightarrow i_L(0^+) = i_L(0^-) = 0A$
 $t \rightarrow \infty \Rightarrow i_L(t \rightarrow \infty) = 4A$ } $\Rightarrow \underline{\underline{i_L(t) = 4[1 - e^{-4t/9}]}}$
 $(t > 0)$

(e)

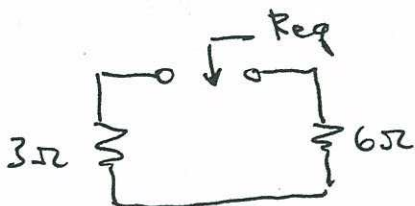

$$\Rightarrow R_{eq} = 3\Omega + 6\Omega = 9\Omega$$

$$\tau = \frac{L}{R} = \frac{4H}{9\Omega} \Rightarrow \underline{\underline{\tau = \frac{4}{9} \text{ sec} \checkmark}}$$

Exercises
chapter 7.5

2. $2 \frac{di(t)}{dt} + 3i(t) = 5v(t)$

DC gain: $\frac{di}{dt} \rightarrow 0 \Rightarrow 3i(t \rightarrow \infty) = 5v(t \rightarrow \infty)$

$$\left. \frac{i(t)}{v(t)} \right|_{t \rightarrow \infty} = \underline{\underline{\frac{5}{3}}}$$



Units are $\frac{A}{V}$.

Time constant: $\frac{di(t)}{dt} + \frac{3}{2}i(t) = \frac{5}{2}v(t)$

$$\uparrow \frac{1}{\tau}$$

$\tau = \underline{\underline{\frac{2}{3} \text{ sec}}}$

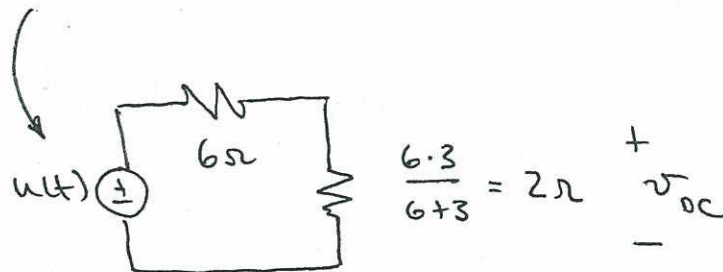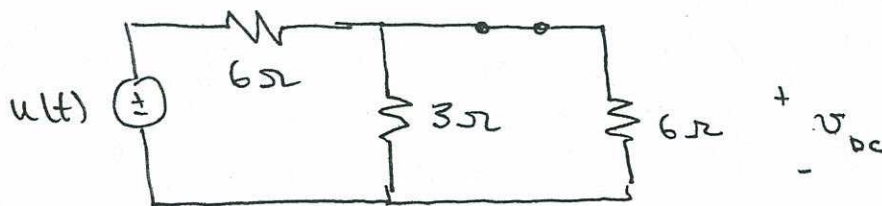3. In steady-state, with $u(t) = \text{constant}$, the inductors becomes a short circuit:




Voltage divider: $v_{oc} = \frac{2}{8}u \Rightarrow \text{DC gain} = \underline{\underline{\frac{1}{4}}}$
units are $\frac{V}{V}$
(unitless)

Exercises
Chapter 7.5

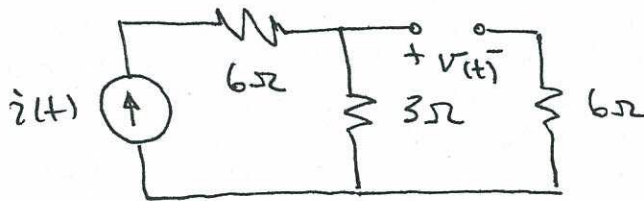4. From differential equation, with $\frac{dv}{dt} = 0$:

$$\frac{1}{9} v(t \rightarrow \infty) = i(t \rightarrow \infty) \Rightarrow \text{DC gain} = 9 \quad (\text{from Diff. eqn.})$$

From circuit, with capacitor open-circuited:




$$v(t) = 3 i(t)$$

$$\Rightarrow \text{D gain} = 3$$

DC gain from circuit different than DC gain from differential equation \Rightarrow D.E. not accurate

5. $3 \frac{dv_c}{dt} + v_c(t) = v(t) \Rightarrow \text{DC gain} = 1$

circuit:

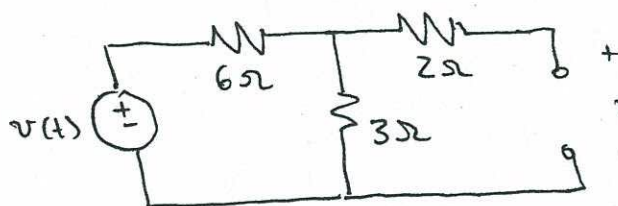

$$\Rightarrow \text{DC gain} = \frac{1}{2}$$

Inconsistent

\Rightarrow Diff. equation probably inaccurate.